

Laboratory Exercise 3

Latches, Flip-flops, and Registers

The purpose of this exercise is to investigate sequential circuits.

Preparation

In advance of your lab period write the Verilog code for Parts I to IV. Also, make sure that you have successfully simulated Parts I to IV with ModelSim. You will need to demonstrate your simulations for some of these parts to your teaching assistant (TA).

In-lab

You are required to complete all parts of the exercise. Your TA will ask you to demonstrate some of these parts.

Part I

Figure 1 depicts a gated RS latch circuit. Verilog code that describes this latch using Boolean logic expressions is given in Figure 2.

 


Figure 1: A gated RS latch circuit.

```
module part1 (Clk, R, S, Qa, Qb);
    input Clk, R, S;
    output Qa, Qb;

    wire R_g, S_g;
    assign R_g = R & Clk;
    assign S_g = S & Clk;
    assign Qa = ~(R_g | Qb);
    assign Qb = ~(S_g | Qa);
endmodule
```

Figure 2: Verilog code for a gated RS latch.

Perform the following:

1. Create a Verilog source-code file for the gated RS latch, using the code in Figure 2.
2. You are to simulate this Verilog code using the input waveforms for *Clk*, *R*, and *S* that are illustrated in Figure 3. You can create these waveforms by making a new ModelSim project and drawing the waves, or by making a Quartus project and then creating a new *University Program VWF* file to simulate within Quartus, or by writing a ModelSim testbench. Sample ModelSim setup files for using a testbench are provided as part of the *design files* for this exercise. Make sure that your simulation results for outputs *Qa* and *Qb* match those depicted in Figure 3, and that you fully understand how the latch circuit works.

 


Figure 3: Simulation waveforms for the gated RS latch.

Part II

Figure 4 shows the circuit for a gated D latch.

 


Figure 4: Circuit for a gated D latch.

Perform the following:

1. Write a Verilog module, named *D_latch*, using the style of code from Figure 2 for the gated D latch.
2. Simulate your gated D latch using the same method that you chose for Part I. Verify that the latch works properly for all input conditions.

- After successfully simulating your gated D latch, use Quartus to implement the latch on the DE1-SoC board. For your Quartus project, you should create a top-level Verilog module, named *part2*, that contains the appropriate input and output ports (pins) for the board. Instantiate your latch in this top-level module. Use switch SW_0 to drive the D input of the latch, and use SW_1 as the Clk input. Connect the Q output to $LEDR_0$.
- Since your *part2.v* file uses the SW switches and LEDR lights on the DE1-SoC board, you may want to simulate your design with the DESim tool. A file *top.v* for use with *DESim* is included with the design files for this exercise. To directly use this *top.v* file, define your *part2.v* module as:

```

module part2 (SW, LEDR);
    input  [1:0] SW;
    output [9:0] LEDR;
    ...
endmodule

```
- After completing simulations of your design, make sure that your Quartus project includes the required pin assignments, then compile the project and download the resulting circuit into the DE1-SoC board.
- Test the functionality of your circuit.

Part III

Figure 5 shows the circuit for a master-slave D flip-flop.

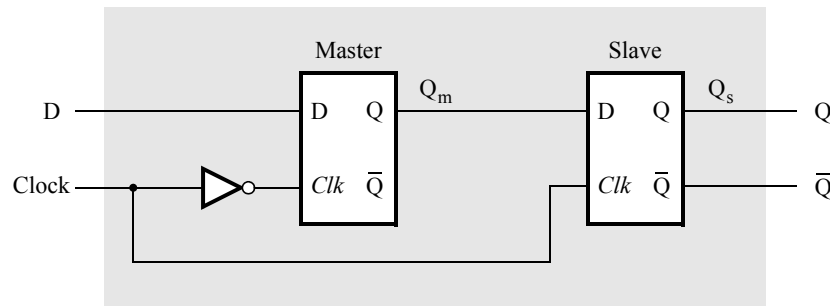


Figure 5: Circuit for a master-slave D flip-flop.

Perform the following:

- Write a Verilog file, named *part3.v*, that instantiates two copies of your gated D latch module from Part II to implement the master-slave flip-flop. Use switch SW_0 to drive the D input of your flip-flop, and use SW_1 as the $Clock$ input. Connect the Q output to $LEDR_0$.
- Simulate your Verilog code using ModelSim. You may want to also simulate your Verilog code with DESim. ModelSim setup files and a *top.v* file for DESim are included with the design files for this exercise.
- After completing simulations of your design, make sure that your Quartus project includes the required pin assignments, then compile the project and download the resulting circuit into the DE1-SoC board.
- Test the functionality of your circuit.

Part IV

Figure 6 illustrates a circuit that includes three different storage elements: a gated D latch, a positive-edge triggered D flip-flop, and a negative-edge triggered D flip-flop.

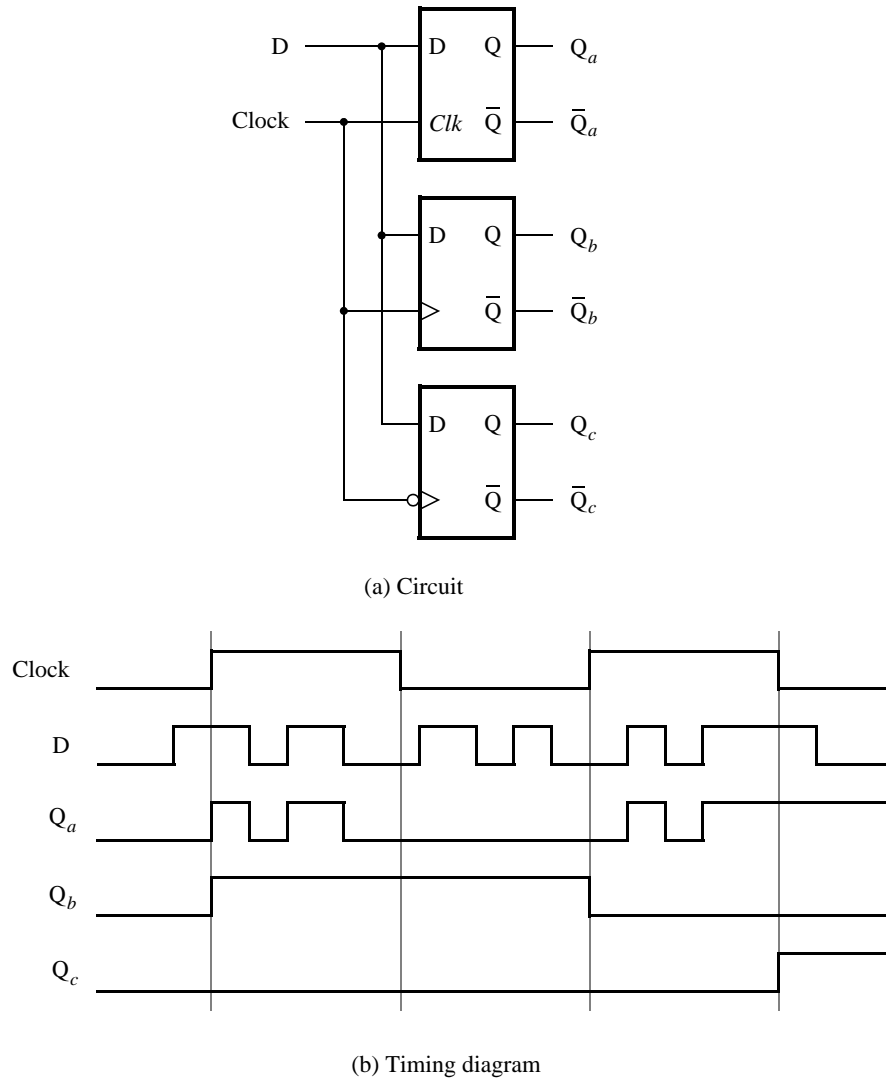


Figure 6: Circuit and waveforms for Part IV.

Perform the following:

1. Write Verilog code that instantiates the three storage elements.
2. Simulate your Verilog code by using ModelSim. You can choose to use ModelSim either by drawing waveforms or using a testbench. For the latter approach, a ModelSim testbench is provided as part of the *design files* for this exercise.

Regardless of your ModelSim methodology, simulate using at least the input waveforms shown for signals *D* and *Clock* in Figure 6. Make sure that you understand the different behaviors of the storage elements.

Part V

We wish to display the hexadecimal value of an 8-bit number A on the two 7-segment displays $HEX3 - 2$. We also wish to display the hex value of an 8-bit number B on the two 7-segment displays $HEX1 - 0$. The values of A and B are inputs to the circuit which are provided by means of switches SW_{7-0} . To input the values of A and B , first set the switches to the desired value of A , store these switch values in a register, and then change the switches to the desired value of B . Finally, use an adder to generate the arithmetic sum $S = A + B$ (the $+$ symbol means *addition* in this expression; it does not mean OR), and display this sum on the 7-segment displays $HEX5 - 4$. Show the carry-out produced by the adder on LEDR[0].

Your Verilog module should be defined as:

```
module part5 (SW, KEY, HEX5, HEX4, HEX3, HEX2, HEX1, HEX0, LEDR);
    input [7:0] SW;
    input [1:0] KEY;
    output [6:0] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
    output [9:0] LEDR;
    ...
    ...
endmodule
```

1. A ModelSim testbench is provided as part of the *design files* for this exercise, as well as a top-level file for use with DESim. Simulation is optional, at your discretion, for this part of the exercise.
2. Create a new Quartus project which will be used to implement the desired circuit on the DE1-SoC board.
3. Write a Verilog file that provides the necessary functionality. Use KEY_0 as an active-low asynchronous reset, and use KEY_1 as a manual clock input.
4. Include the necessary pin assignments for the switches and 7-segment displays, and then compile the circuit.
5. Download your circuit into the DE1-SoC board and test its functionality by operating the switches and observing the displays.